

Part 1

The design explanation:

My design is a digital calendar which display (day , month , year) in base-19 on 7-segment

Using CD4024 - 7-Bit Binary Counter and

With digital clock generator of period “ 24hours “

And Settable digits for each element

Special case in February ends at 28

Correction circuit :

Which are the blocks {DAY DIGIT1, DAY DIGIT2, MONTH , YEAR DIGIT1 , YEAR DIGIT2 , YEAR DIGIT3}

They're all -binary-to-base 19 ' seven segment decoders

- First digit of day “check the value 19 (Bin 10010) and reset and increase second digit of day
 - Check 30 day which means (1B) in base-19 and then reset both digits and increase month first digit by 1
 - Special case on February (check month value 2) & check value of day with value 28 (19 in base-19) then reset both the days digits
 - Same thing at year digits it resets every 19 “I” (10010)
-

The design main functions :

First function is the clock “pulse generator “ and every day “24 hours “ gives a signal

Second is to read and count these pulses then decode it to binary

after that step there are two steps in parallel :


1. encoding the binary input to output coded 7 segment code
2. checking the value of the binary code to reset the first digit and give signal to increase the 2nd digit by 1

then check the both digits of value of 30 days which is (1b) in base-19 system which is displayed on the 7-segments

then increase the month digits by 1 .

same process goes to the month digit until it's 12 months which is (C) in base-19 system displayed on 7-segment and then increase year digits by 1 etc....

Use case of the design :

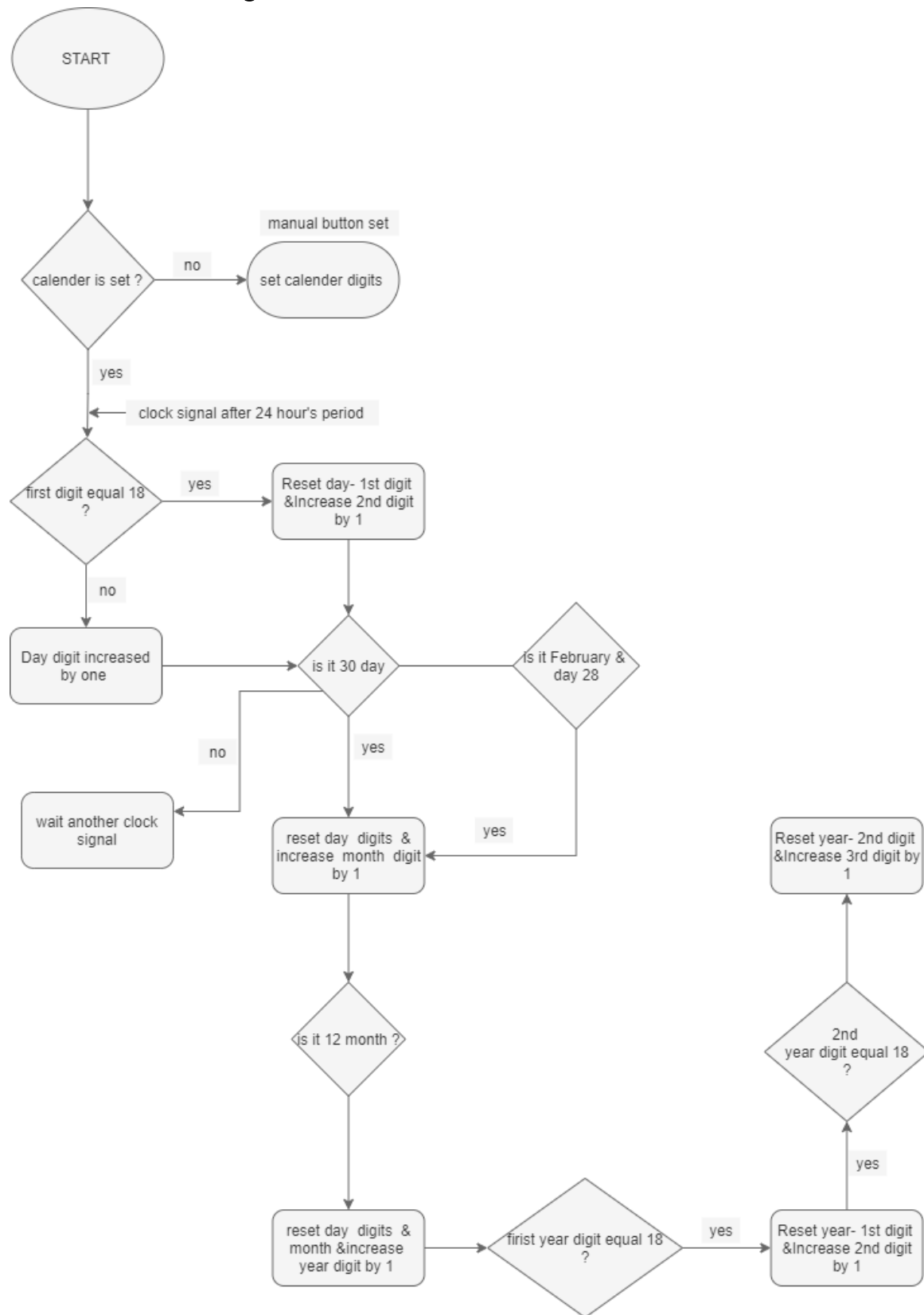

List of components used in design :

Active components :

Dc generator 5v	To supply my manual set of digits for each day , month and year
Digital clock generator with period 86,400 second	To represent my clock of da 24 hours
Logic gates (OR"7432" , AND" 74ls08",NOT" 7404")	For the logical design and Equations representation
CD4024 - 7-Bit Binary Counter	To count my clock signals and the o/p is easier to be handled
7-segment	To display the output

passive components :

1n4007 diode	To prevent the flow of current in the reverse direction
Resistors (330 , 10k) ohm	Circuit requirement
Ground	
Buttons	To manual set and connect a pulse as a manual clock

General idea

Each block of blocks {DAY DIGIT1, DAY DIGIT2, MONTH , YEAR DIGIT1 , YEAR DIGIT2 , YEAR DIGIT3}


Are same design which means same input and same output :
inputs are the numbers in 5 bits in binary : <<< **I1 I2 I3 I4 I5** >>>


Outputs are the encoded 7-segment code portable for **base-19** : <<< **A B C D E F G** >>>

*note : in design for design issues I had to change names

Inputs to A -B-C-D-E

Outputs to aa-bb-cc-dd-ee-ff-gg

 

Binary Input $i_1 i_5$		Decimal	A o/p ₁	B o/p ₂	C o/p ₃	D o/p ₄	E o/p ₅	F o/p ₆	G o/p ₇
00000	0	0	1	1	1	1	1	1	0
00001	1	1	0	1	1	0	0	0	0
00010	2	2	1	1	0	1	1	0	1
00011	3	3	1	1	1	1	0	0	1
00100	4	4	0	1	1	0	0	1	1
00101	5	5	1	0	1	1	0	1	1
00110	6	6	1	0	1	1	1	1	1
00111	7	7	1	1	1	0	0	0	0
01000	8	8	1	1	1	1	1	1	1
01001	9	9	1	1	1	1	0	1	1
01010	a	10	1	1	1	1	1	0	1
01011	b	11	0	0	1	1	1	1	1
01100	c	12	1	0	0	1	1	1	0
01101	d	13	0	1	1	1	1	0	1
01110	e	14	1	1	0	1	1	1	1
01111	f	15	1	0	0	0	1	1	1
10000	g	16	1	1	1	1	0	1	1
10001	h	17	0	0	1	0	1	1	1
10010	i	18	0	0	0	0	1	1	0

“A” K map of design:

A	$i_2' . l_1'$	$i_2' . i_1$	$l_2 . i_1$	$l_2 . i_1'$
$l_5' . l_4 . i_3$	1	1	1	1
$l_5' . i_4' . i_3$	1	0	1	0
$l_5' . i_4 . i_3$	0	1	0	1
$l_5' . i_4 . i_3'$	1	1	0	1
$l_5 . i_4' . i_3'$	1	0	x	0
$l_5 . i_4' . i_3$	x	x	x	x
$l_5 . i_4 . i_3$	x	x	x	x
$l_5 . i_4 . i_3'$	x	x	x	x

The equation of A:

$$A = l_1' l_2' l_3' + l_1' l_3' l_4' + l_2' l_4' l_5' + l_2' l_4 l_5 + l_2 l_4' l_5 + l_2 l_4 l_5'$$

K map of design:

B	$i_2' . l_1'$	$i_2' . i_1$	$l_2 . i_1$	$l_2 . i_1'$
$l_5' . l_4 . i_3$	1	1	1	1
$l_5' . i_4' . i_3$	1	0	1	0
$l_5' . i_4 . i_3$	0	1	0	1
$l_5' . i_4 . i_3'$	1	1	0	1
$l_5 . i_4' . i_3'$	1	0	x	0
$l_5 . i_4' . i_3$	x	x	x	x
$l_5 . i_4 . i_3$	x	x	x	x
$l_5 . i_4 . i_3'$	x	x	x	x

The equation of B:

$$B = l_5' . i_4 . i_3' + l_5' . i_3' . i_2' + l_2' . i_2' . i_1' + i_4' . i_2 . i_1 + i_4 . i_2' . i_1 + i_4 . i_2 . i_1'$$

“C” K map of design:

C	$l_4' . l_5'$	$l_4' . i_5$	$l_4 . i_5$	$l_4 . i_5'$
$l_1' . l_2' . i_3'$	1	1	1	0
$l_1' . i_2' . i_3$	1	1	1	1
$l_1' . i_2 . i_3$	0	1	0	0
$l_1' . i_2 . i_3'$	1	1	1	1
$l_1 . i_2' . i_3'$	1	1	x	0
$l_1 . i_2' . i_3$	x	x	x	x
$l_1 . i_2 . i_3$	x	x	x	x
$l_1 . i_2 . i_3'$	x	x	x	x

The equation of C:

$$C = l_2' l_4' + l_2' l_5 + l_4' l_5 + l_2' l_3 + l_2 l_3'$$

“D” K map of design:

D	$l_4' . l_5'$	$l_4' . i_5$	$l_4 . i_5$	$l_4 . i_5'$
$l_1' . l_2' . i_3'$	1	0	1	1
$l_1' . i_2' . i_3$	0	1	0	1
$l_1' . i_2 . i_3$	1	1	0	1
$l_1' . i_2 . i_3'$	1	1	1	1
$l_1 . i_2' . i_3'$	1	0	x	0
$l_1 . i_2' . i_3$	x	x	x	x
$l_1 . i_2 . i_3$	x	x	x	x
$l_1 . i_2 . i_3'$	x	x	x	x

The equation of D:

$$D = l_2 l_4' + l_1' l_3' l_4' + l_1' l_4 l_5' + l_3' l_4' l_5' + l_3 l_4' l_5$$

“E” K map of design:

E	$l_4' . l_5'$	$l_4' . i_5$	$l_4 . i_5$	$l_4 . i_5'$
$l_1' . l_2' . i_3'$	1	0	0	1
$l_1' . i_2' . i_3$	0	0	0	1
$l_1' . i_2 . i_3$	1	1	1	1
$l_1' . i_2 . i_3'$	1	0	1	0
$l_1 . i_2' . i_3'$	0	1	x	0
$l_1 . i_2' . i_3$	x	x	x	x
$l_1 . i_2 . i_3$	x	x	x	x
$l_1 . i_2 . i_3'$	x	x	x	x

The equation of E:

$$E = l_2 l_3 + l_1 l_5 + l_2' l_4 l_5' + l_2 l_4 l_5 + l_1' l_3' l_4' l_5'$$

“F” K map of design:

F	$l_4' . l_5'$	$l_4' . i_5$	$l_4 . i_5$	$l_4 . i_5'$
$l_1' . l_2' . i_3'$	1	0	0	0
$l_1' . i_2' . i_3$	1	1	0	1
$l_1' . i_2 . i_3$	1	0	1	1
$l_1' . i_2 . i_3'$	1	1	1	1
$l_1 . i_2' . i_3'$	1	1	x	1
$l_1 . i_2' . i_3$	x	x	x	x
$l_1 . i_2 . i_3$	x	x	x	x
$l_1 . i_2 . i_3'$	x	x	x	x

The equation of F:

$$F = l_1 + l_4' l_5' + l_3 l_5' + l_2 l_3' + l_2 l_4 + l_2' l_3 l_4'$$

“G” K map of design:


G	$l_4' . l_5'$	$l_4' . i_5$	$l_4 . i_5$	$l_4 . i_5'$
$l_1' . l_2' . i_3'$	0	0	1	1
$l_1' . i_2' . i_3$	1	1	0	1
$l_1' . i_2 . i_3$	0	1	1	1
$l_1' . i_2 . i_3'$	1	1	1	1
$l_1 . i_2' . i_3'$	1	1	x	0
$l_1 . i_2' . i_3$	x	x	x	x
$l_1 . i_2 . i_3$	x	x	x	x
$l_1 . i_2 . i_3'$	x	x	x	x

The equation of G:


$$G = l_2 l_3' + l_2 l_5 + l_1 l_4' + l_1' l_3' l_4 + l_1' l_4 l_5' + l_2' l_3 l_4'$$

EXAMPLES

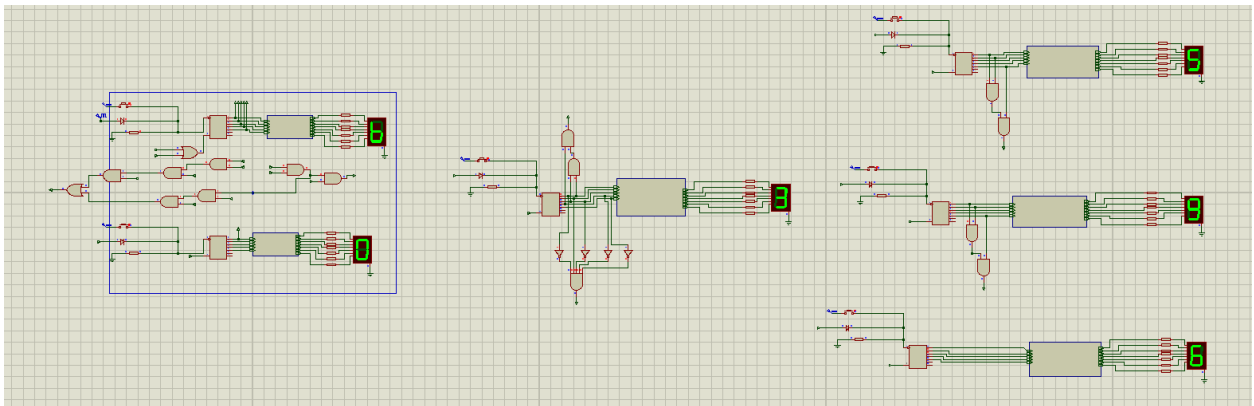
Example (1) : >>12/3/ 1982 -----> b/3/596



 
Example (2) : >>10/6/ 2020 -----> a/6/5b6



 
Example (3) : >>28/5/ 1997 -----> 19/5/ 5a2



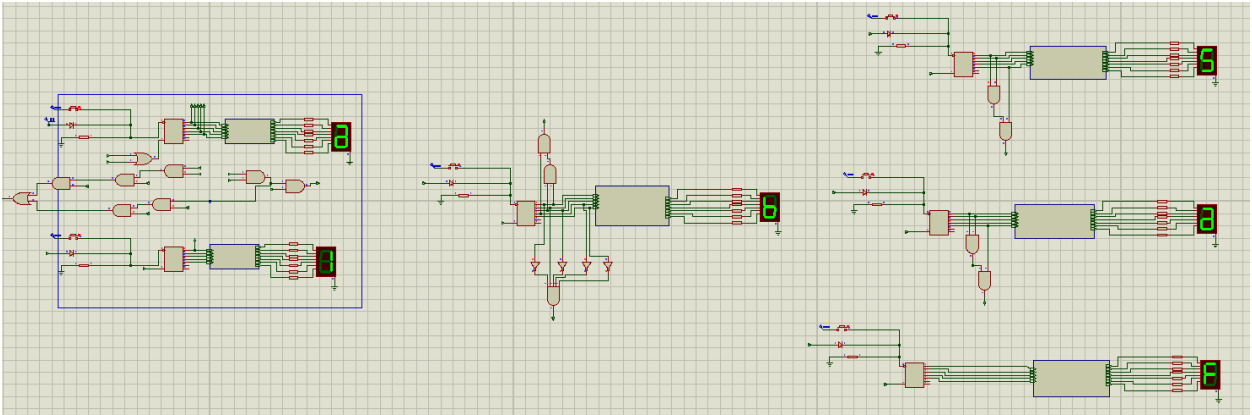Example (4) : >>29/11/ 2019 -----> 1a/b/ 5af



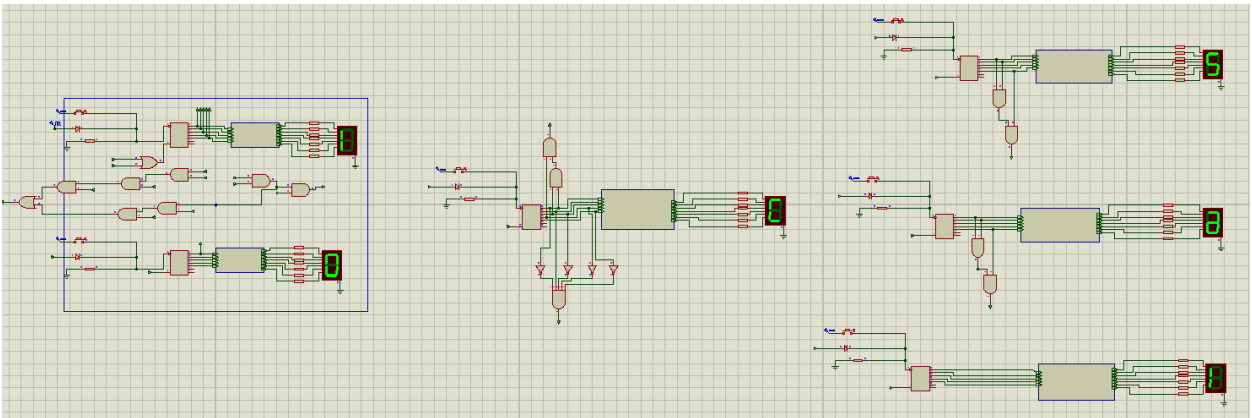Example (5) : >>18/12/ 2013 -----> 10/b/ 5a1



***NOTE:**

1 → 18	1 → 1